

Final exam for CMPE 3403 (Electronics for Computer Engineering)

1:15pm-3:00pm 5/5/2020

You have 15 minutes for uploading your answer sheets to Blackboard, so please finish uploading by 3:15pm.

Name: _____, ID#: _____

Note: this exam is an online exam with open-book and open-notes. For your convenience of uploading, you can write your solutions (including reasonable details) on papers and scan/take pictures, upload to Blackboard in the same way as you did for homework assignments. **Please be sure to write your name, and ID# on the first page of your submission,** and to submit your work to Blackboard **by 3:15 pm.**

I. Multiple Choice (30 points)

1. The i - v curve of the diode in Fig.1(a) is plotted in Fig.1.(b), then the value of v_o in Fig.1(a) is

- a) 0 V
- b) 0.5 V
- c) 1 V
- d) 10 V

 


Fig.1 (a)

 


Fig.1 (b)

2. The 3D structure of a MOSFET is shown in Fig.2. The channel width of the transistor is
- a) 1.8 μm
 - b) 0.18 μm
 - c) Not shown
 - d) Could be any

 


Fig.2 the structure of a transistor

3. The voltage gain of the circuit in Fig.3 is defined as v_o/v_i . What is the voltage gain?

- a) 1
- b) 2
- c) 3
- d) 4

 


Fig.3

4. In Fig.3, the value of i_o is

- a) 1 mA
- b) 2 mA
- c) 3 mA
- d) 4 mA

5. The PMOS transistor has $V_{tp} = -1\text{ V}$. If the voltages of three terminals are: $V_g = 2\text{ V}$, $V_s = 5\text{ V}$, $V_d = 1\text{ V}$, then the transistor is operated in
- Cut off region
 - Triode region
 - Saturation region
 - Unknown

6. The voltage transfer characteristic of a CMOS inverter is shown in Fig.4. Threshold voltages $V_{tn} = |V_{tp}| = 0.5\text{ V}$. If the input $v_i = 1\text{ V}$, then

- Both PMOS and NMOS in triode region
- Both PMOS and NMOS in saturation
- PMOS in triode region, and NMOS in saturation
- PMOS in saturation, and NMOS in triode

 


Fig. 4

- II. (20 points) For the circuit in Fig.5, find the value of R that results in $V_D = 1\text{ V}$. The PMOS transistor has $V_{tp} = -0.5\text{ V}$, $\mu_p C_{ox} = 100\text{ uA/V}^2$, $W/L = 7.2\text{ um}/0.18\text{ um}$, and $\lambda = 0$.

 


Fig.5

III. (20 points) Logic gate design at transistor level:

- 1) Find the Pull-up network (PUN) that corresponds to the Pull-down network (PDN) shown in Fig.6.
- 2) Draw the complete CMOS logic circuit using the PUN and PDN.
- 3) Find the logic function for the circuit you derived in 2).

 


Fig.6

IV. (30 points) The circuit in Fig.7 utilizes an ideal operational amplifier.

- a) Find I_1 , I_2 , I_3 , I_L , and V_x .
- b) If V_o is not to be lower than -13 V, find the maximum allowed value for R_L .
- c) If R_L is varied in the range $100\ \Omega$ to $1\ \text{k}\Omega$, what is the corresponding change in I_L and in V_o ?

 


Fig.7